
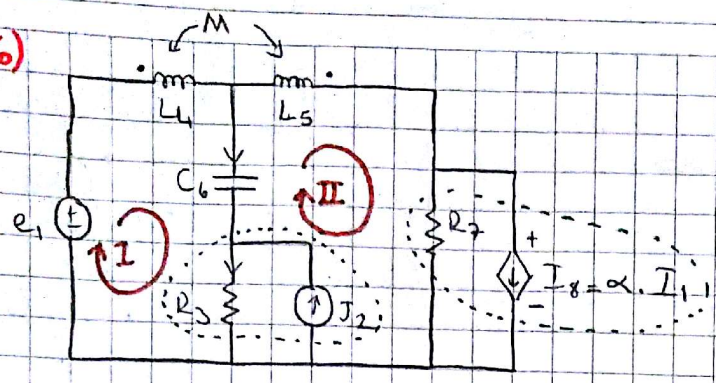


6)

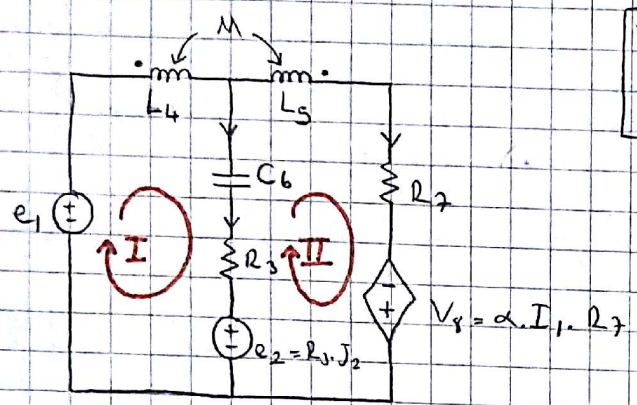

Başlangıç değerleri  $\neq 0$ . Gösterilen çevreleri  $s$  bölgesinde yazınız.

$$X = \begin{bmatrix} I_{c1} \\ I_{c2} \end{bmatrix}$$



$$\begin{bmatrix} V_4(s) \\ V_5(s) \end{bmatrix} = s \begin{bmatrix} L_4 & -M \\ -M & L_5 \end{bmatrix} \begin{bmatrix} I_4(s) \\ I_5(s) \end{bmatrix} - \begin{bmatrix} L_4 & -M \\ -M & L_5 \end{bmatrix} \begin{bmatrix} I_4(t_0) \\ I_5(t_0) \end{bmatrix}$$

$$V_4(s) = s \cdot L_4 I_4(s) - L_4 I_4(t_0) - s M I_5(s) + M I_5(t_0)$$

$$V_5(s) = -s M I_4 + M I_4(t_0) + s L_5 I_5 - L_5 I_5(t_0)$$

I)  $-V_1 + V_4 + V_6 + V_3 + V_2 = 0$

II)  $-V_2 - V_3 - V_6 + V_5 + V_7 - V_8 = 0$

2) I)  $-E_1(s) + sL_4 I_4(s) - L_4 I_4(t_0) - sM I_5(s) + M I_5(t_0) + \frac{1}{sC_6} (I_4(s) - I_4(t_0)) + R_3 I_3(s) + R_3 J_2(s) = 0$

II)  $-R_3 J_2(s) - R_3 I_3(s) - \frac{1}{sC_6} (I_4(s) - I_4(t_0)) - \frac{V_6(t_0)}{s} - sM I_4 + M I_4(t_0) + sL_5 I_5 - L_5 I_5(t_0) + R_7 I_7(s) - \alpha \cdot I_1 \cdot R_7 = 0$

3)  $I_3 = I_{c1} - I_{c2}$ ,  $I_4 = I_{c1}$ ,  $I_5 = I_{c2}$ ,  $I_6 = I_{c1} - I_{c2}$ ,  $I_7 = I_{c2}$ ,  $I_1 = -I_{c1}$

I)  $-E_1 + sL_4 I_{c1} - L_4 I_4(t_0) - sM I_{c2} + M I_5(t_0) + \frac{1}{sC_6} (I_{c1} - I_{c2}) + \frac{V_6(t_0)}{s} + R_3 (I_{c1} - I_{c2}) + R_3 J_2(s) = 0$

II)  $-R_3 J_2(s) - R_3 (I_{c1} - I_{c2}) - \frac{1}{sC_6} (I_{c1} - I_{c2}) - \frac{V_6(t_0)}{s} - sM I_{c1} + M I_4(t_0) + sL_5 I_{c2} - L_5 I_5(t_0) + R_7 I_{c2} + \alpha I_{c1} R_7 = 0$


4)

$$\begin{bmatrix} I \\ II \end{bmatrix} \begin{bmatrix} sL_4 + \frac{1}{sC_6} + R_3 & -sM - \frac{1}{sC_6} - R_3 \\ -R_3 - \frac{1}{sC_6} - sM + \alpha R_7 & R_3 + \frac{1}{sC_6} + sL_5 + R_7 \end{bmatrix} \begin{bmatrix} I_{c1}(s) \\ I_{c2}(s) \end{bmatrix} = \begin{bmatrix} E_1(s) - R_3 J_2(s) \\ R_3 J_2(s) \end{bmatrix} + \begin{bmatrix} L_4 I_4(t_0) - M I_5(t_0) - \frac{V_6(t_0)}{s} \\ \frac{V_6(t_0)}{s} - M I_4(t_0) + L_5 I_5(t_0) \end{bmatrix}$$

$Z_c(s)$  = bağımsız çevre empedans matrisi
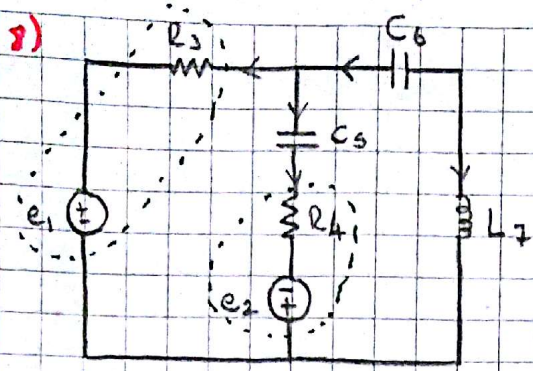
$$I_c = E(s) + \text{Başlangıç değerleri}$$






Temel kesitlere denklemleri ile söz.

$$n = 4 \quad \text{dal} = n - 1 = 3$$
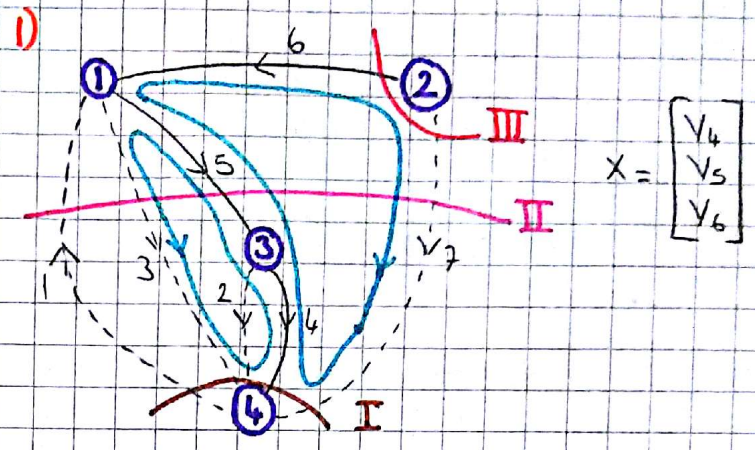
$$n_e = 7 \quad \text{kuris} = n_e - n + 1 = 4$$



2) I)  $-I_1 + I_3 + I_2 + I_4 + I_7 = 0$

II)  $-I_1 + I_3 + I_5 + I_7 = 0$

III)  $I_7 + I_6 = 0$

3) I)  $-\frac{E_1(s)}{R_3} + G_3 V_3 + \frac{E_2(s)}{R_4} + G_4 V_4 + \frac{1}{sL_7} V_7(s) + \frac{I_7(t_0)}{s} = 0$

$$V_3 = V_4 + V_5$$

$$V_7 = V_4 + V_5 + V_6$$

II)  $-\frac{E_1(s)}{R_3} + G_3 V_3 + sC_5 V_5(s) - C_5 V_5(t_0) + \frac{1}{sL_7} V_7(s) + \frac{I_7(t_0)}{s} = 0$

III)  $\frac{1}{sL_7} V_7(s) + \frac{I_7(t_0)}{s} + sC_6 V_6(s) - C_6 V_6(t_0) = 0$


I)  $-\frac{E_1(s)}{R_3} + G_3 V_4 + G_3 V_5 + \frac{E_2(s)}{R_4} + G_4 V_4 + \frac{1}{sL_7} (V_4 + V_5 + V_6) + \frac{I_7(t_0)}{s} = 0$

II)  $-\frac{E_1(s)}{R_3} + G_3 (V_4 + V_5) + sC_5 V_5(s) - C_5 V_5(t_0) + \frac{1}{sL_7} (V_4 + V_5 + V_6) + \frac{I_7(t_0)}{s} = 0$

III)  $\frac{1}{sL_7} (V_4 + V_5 + V_6) + \frac{I_7(t_0)}{s} + sC_6 V_6(s) - C_6 V_6(t_0) = 0$

I	$G_3 + G_4 + \frac{1}{sL_7}$	$G_3 + \frac{1}{sL_7}$	$\frac{1}{sL_7}$	$V_4$	$= \begin{bmatrix} \frac{E_1(s)}{R_3} - \frac{E_2(s)}{R_4} \\ \frac{E_1(s)}{R_3} \\ 0 \end{bmatrix} + \begin{bmatrix} -\frac{I_7(t_0)}{s} \\ C_5 V_5(t_0) - \frac{I_7(t_0)}{s} \\ C_6 V_6(t_0) - \frac{I_7(t_0)}{s} \end{bmatrix}$
II	$G_3 + \frac{1}{sL_7}$	$G_3 + sC_5 + \frac{1}{sL_7}$	$\frac{1}{sL_7}$	$V_5$	
III	$\frac{1}{sL_7}$	$\frac{1}{sL_7}$	$\frac{1}{sL_7} + sC_6$	$V_6$	

10)

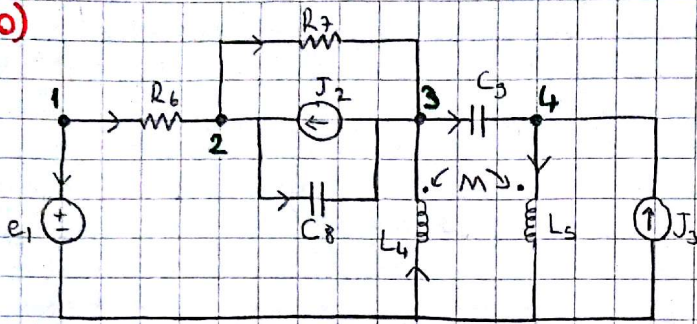

Düğün denklemleri yöntemiyle çözün.

$$X = \begin{bmatrix} I_1 \\ V_{d1} \\ V_{d2} \\ V_{d3} \\ V_{d4} \end{bmatrix} \quad V_{d1} = e_1$$

1)

$$\begin{bmatrix} V_4 \\ V_5 \end{bmatrix} = s \begin{bmatrix} L_4 & -M \\ -M & L_5 \end{bmatrix} \begin{bmatrix} I_4 \\ I_5 \end{bmatrix} - \begin{bmatrix} L_4 & -M \\ -M & L_5 \end{bmatrix} \begin{bmatrix} I_{4(t_0)} \\ I_{5(t_0)} \end{bmatrix} \quad \begin{bmatrix} I_4 \\ I_5 \end{bmatrix} = \begin{bmatrix} L_5/\Delta_s & M/\Delta_s \\ M/\Delta_s & L_4/\Delta_s \end{bmatrix} \begin{bmatrix} V_4 \\ V_5 \end{bmatrix} + \begin{bmatrix} I_{4(t_0)}/s \\ I_{5(t_0)}/s \end{bmatrix}$$

2) I)  $I_6 + I_1 = 0$

II)  $-I_2 - I_6 + I_7 + I_8 = 0$

III)  $I_2 - I_8 - I_7 + I_5 - I_4 = 0$

IV)  $-I_3 + I_5 - I_3 = 0$

3) I)  $I_1 + G_6 \cdot V_6 = 0$

II)  $-J_2 - G_6 V_6 + G_7 V_7 + s C_8 V_8(s) - C_8 V_8(t_0) = 0$

III)  $J_2 - s C_8 V_8(s) + C_8 V_8(t_0) - G_7 V_7 + s C_3 V_3(s) - C_3 V_3(t_0) - \frac{L_5}{\Delta_s} V_4 - \frac{M}{\Delta_s} V_5 - \frac{I_{4(t_0)}}{s} = 0$

IV)  $-s C_3 V_3 + C_3 V_3(t_0) + \frac{M}{\Delta_s} V_4 + \frac{L_4}{\Delta_s} V_5 + \frac{I_{4(t_0)}}{s} - J_3 = 0$

$V_4 = -V_{d3}, V_5 = V_{d4}, V_6 = V_{d1} - V_{d2} = e_1 - V_{d2}, V_7 = V_{d2} - V_{d3}, V_8 = V_{d2} - V_{d3}, V_3 = V_{d3} - V_{d4}$

I)  $I_1 + G_6(e_1 - V_{d2}) = 0$

II)  $-J_2 - G_6(e_1 - V_{d2}) + G_7(V_{d2} - V_{d3}) + s C_8(V_{d2} - V_{d3}) - C_8 V_8(t_0) = 0$

III)  $J_2 - s C_8(V_{d2} - V_{d3}) + C_8 V_8(t_0) - G_7(V_{d2} - V_{d3}) + s C_3(V_{d3} - V_{d4}) - C_3 V_3(t_0) + \frac{L_5}{\Delta_s} V_{d3} - \frac{M}{\Delta_s} V_{d4} - \frac{I_{4(t_0)}}{s} = 0$

IV)  $s C_3(V_{d3} - V_{d4}) + C_3 V_3(t_0) - \frac{M}{\Delta_s} V_{d3} + \frac{L_4}{\Delta_s} V_{d4} + \frac{I_{4(t_0)}}{s} - J_3 = 0$

4)

	$I_1$	$V_{d2}$	$V_{d3}$	$V_{d4}$			
1	1	$-G_6$	0	0	$\begin{bmatrix} I_1 \\ V_{d2} \\ V_{d3} \\ V_{d4} \end{bmatrix} = \begin{bmatrix} -G_6 E_1(s) \\ -G_6 E_1(s) + J_2(s) \\ -J_2(s) \\ J_3(s) \end{bmatrix} + \begin{bmatrix} 0 \\ C_8 V_8(t_0) \\ -C_8 V_8(t_0) + C_9 V_9(t_0) + \frac{I_4(t_0)}{s} \\ -C_9 V_9(t_0) - \frac{I_4(t_0)}{s} \end{bmatrix}$		
2	0	$G_6 + G_7 + sC_8$	$-G_7 - sC_4$	0			
3	0	$-sC_8 - G_7$	$sC_8 + G_7 + sC_9 + \frac{Ls}{\Delta_s}$	$-\frac{M}{\Delta_s} sC_9$			
4	0	0	$-sC_9 - \frac{M}{\Delta_s}$	$sC_9 + \frac{L_4}{\Delta_s}$			