

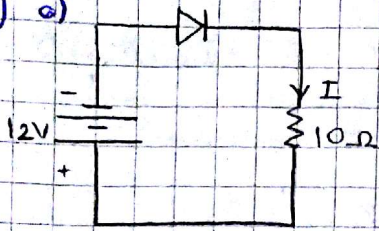


5) a)

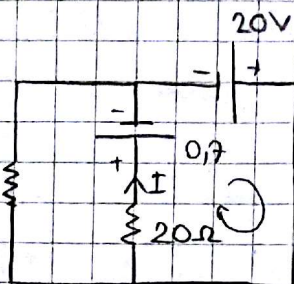

diyot ters kutuplanıy $I = 0 \text{ A}$



b)

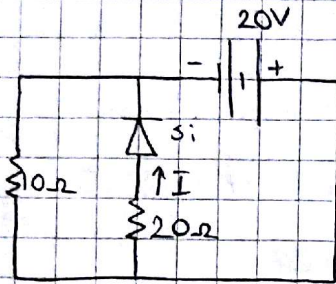

$$-20 + I \cdot 20 + 0.7 = 0$$

$$\frac{19.3}{20} = I = 0.965 \text{ A}$$

6) a)

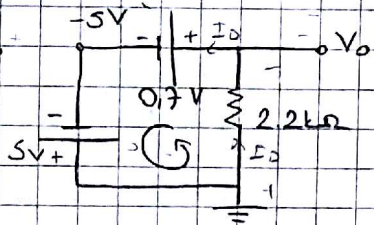
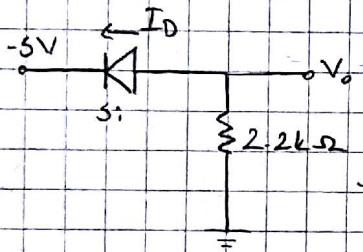


$$-5V + I_D \cdot 2200 + 0.7 = 0$$

$$I_D = 1.855 \text{ mA}$$

$$V_o = V_R = -4.3 \text{ V}$$

b)

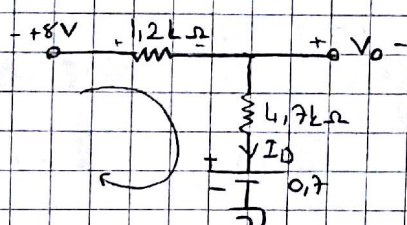
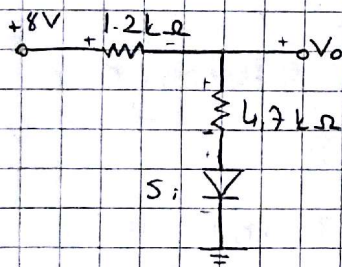


$$-8V + I_D \cdot 1.2k\Omega + I_D \cdot 4.7k\Omega + 0.7 = 0$$

$$I_D = 1.24 \text{ mA}$$



$$V_o = 4.7k\Omega \cdot 1.24 \text{ mA} + 0.7 = 6.53 \text{ V}$$

a)

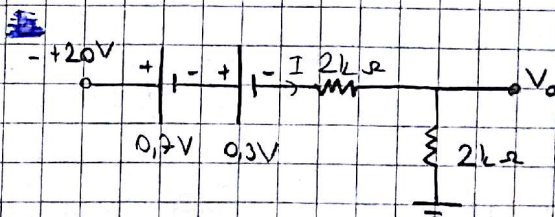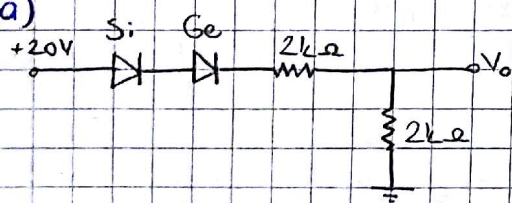

$$-20V + 0.7 + 0.3 + I \cdot 4k\Omega = 0 \quad 4.75 \text{ mA} \quad V_o = 2k\Omega \cdot 4.75 \text{ mA} \quad \underline{V_o = 9.5 \text{ V}}$$


b)

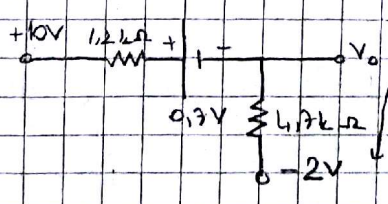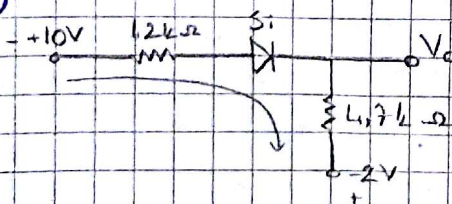


$$-10 + I \cdot 1.2k\Omega + 0.7 + I \cdot 4.7k\Omega - 2 = 0$$

$$I = 1.815 \text{ mA}$$
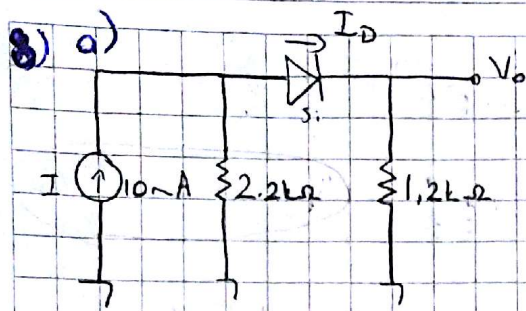
$$V_o = I \cdot 4.7k\Omega - 2 = 7 \text{ V}$$




$$V = I \cdot R = 22V$$

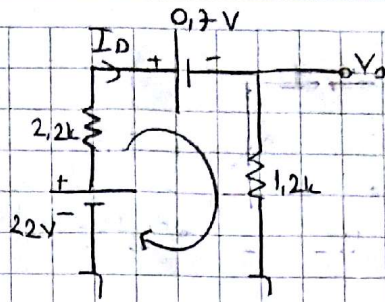

$$-22 + I_D \cdot 2.2k + 0.7 + I_D \cdot 1.2k = 0$$

$$I_D = 6.26 \text{ mA}$$




$$V_o = I_D \cdot 1.2k = 7.51V$$

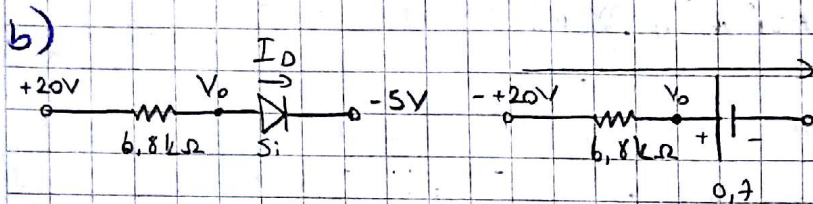

$$-20 + I_D \cdot 6.8k + 0.7 - 5 = 0$$

$$I_D = 3.57 \text{ mA}$$

$$V_o = 0.7 - 5 = -4.3V$$

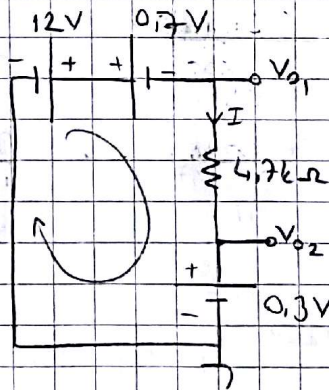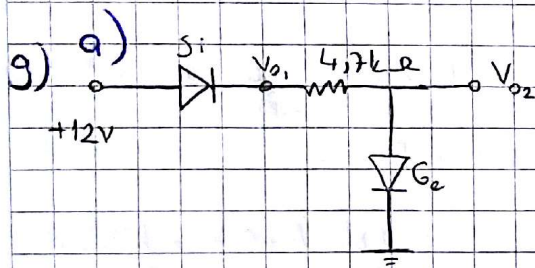
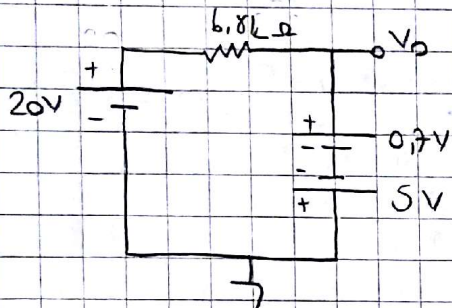


$$-12 + 0.7 + I \cdot 4.7k + 0.3 = 0$$

$$I = 2.34 \text{ mA}$$

$$V_{o1} = I \cdot 4.7k + 0.3 = 11.3V$$

$$V_{o2} = 0.3V$$

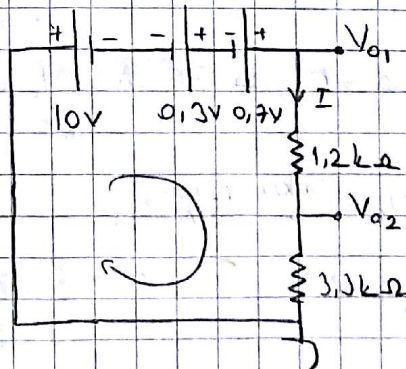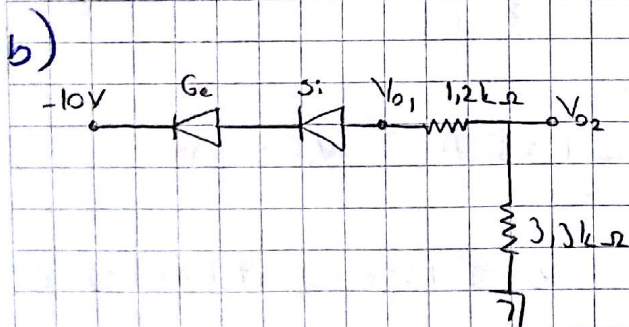



$$10 - 0.3 - 0.7 + I \cdot 1.2k + I \cdot 3.3k = 0$$

$$I = 2 \text{ mA}$$

$$V_{o1} = -5V$$

$$V_{o2} = I \cdot 3.3k = -6.6V$$

10) a)

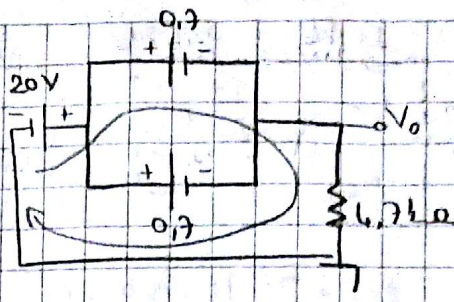
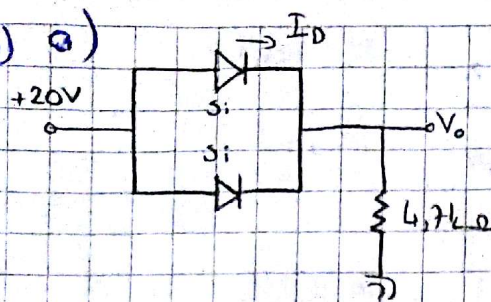


$$-20 + 0.7 + I_D \cdot 4.7k = 0$$

$$I_D = 4.1 \text{ mA}$$

$$V_o = I_D \cdot 4.7k = 19.27 \text{ V}$$

b)

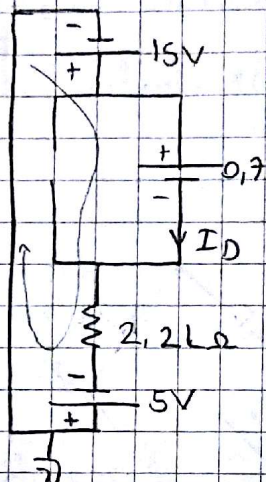
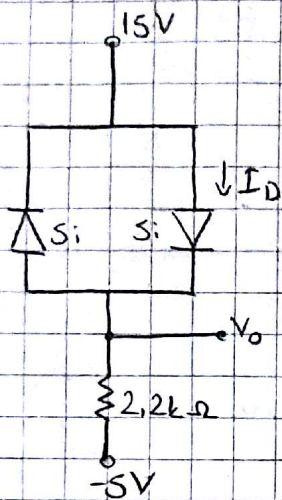


$$-15 + 0.7 + I_D \cdot 2.2k - 5 = 0$$

$$I_D = 8.77 \text{ mA}$$

$$V_o = I_D \cdot 2.2k - 5V = 14.234 \text{ V}$$

11) a)

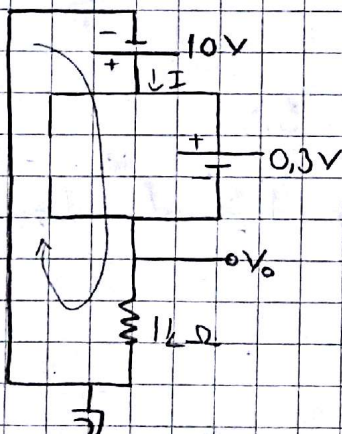
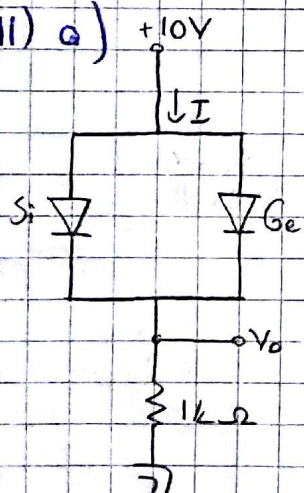


$$-10 + 0.7 + I \cdot 1k = 0$$

$$I = 9.7 \text{ mA}$$

$$V_o = I \cdot 1k = 9.7 \text{ V}$$

b)

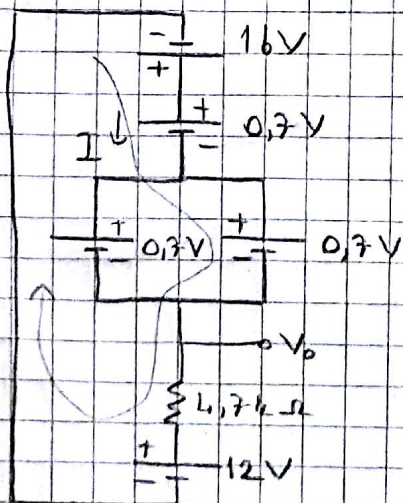
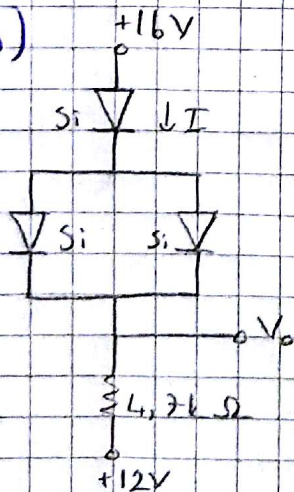


$$-16 + 0.7 + 0.7 + I \cdot 4.7k + 12 = 0$$

$$I = 0.553 \text{ mA}$$

$$V_o = I \cdot 4.7k + 12 = 14.553 \text{ V}$$

12)

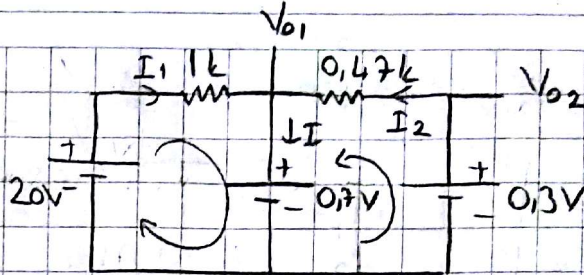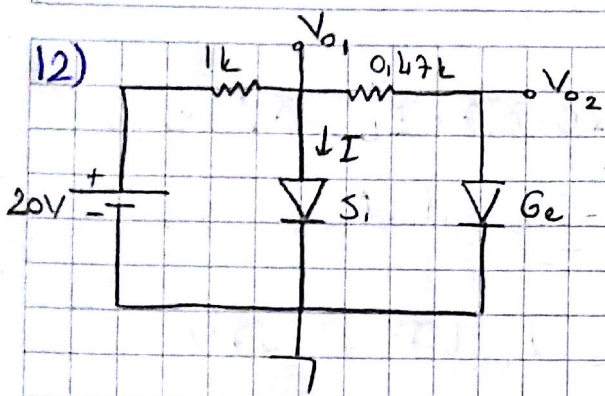

$$V_{01} = 0,7V$$



$$V_{02} = 0,3V$$

$$-20 + I_1 \cdot 1k + 0,7 = 0 \quad I_1 = 18,3 \mu A$$

$$-0,3 + I_2 \cdot 0,47k + 0,7 = 0 \quad I_2 = -0,851 \mu A$$



$$I = 18,3 - 0,851 = 18,45 \mu A$$

13)



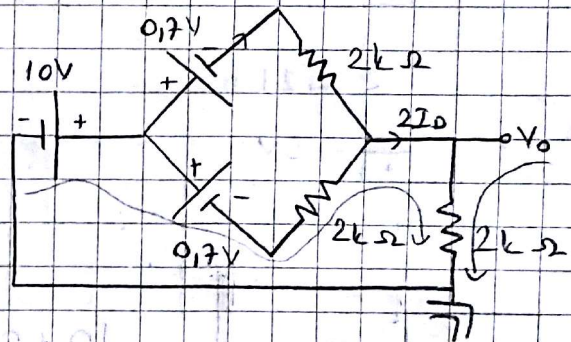
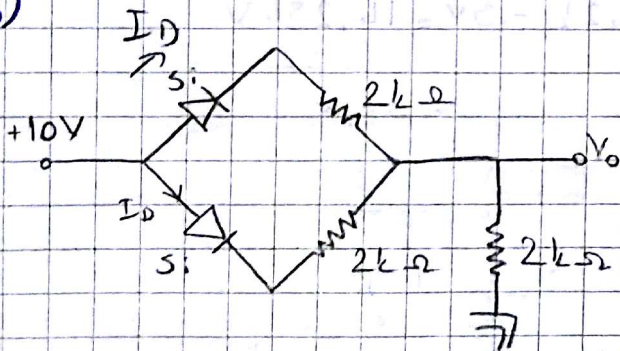


$$-10 + 0,7 + I_0 \cdot 2000 + 2I_0 \cdot 2000 = 0 \quad 6000I_0 = 9,3$$
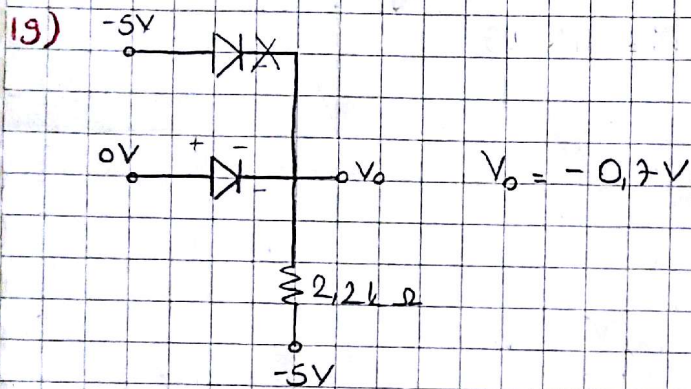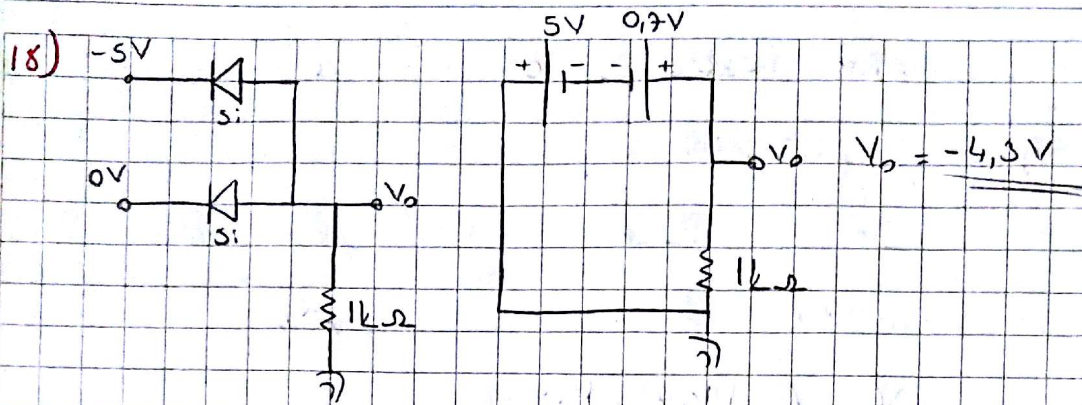
$$V_0 = 2I_0 \cdot 2000 = 4000I_0 \quad V_0 = 6,2V \quad I_0 = 1,55 \mu A \quad I_{2k} = 3,1 \mu A$$



Yom delgo

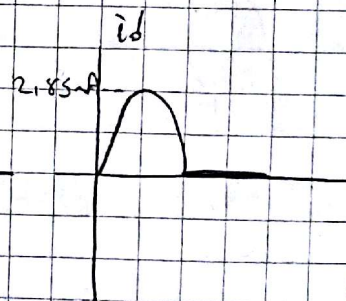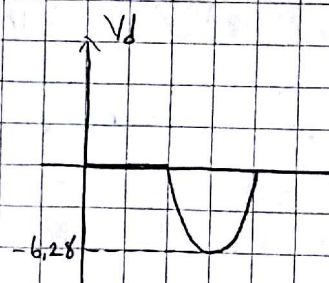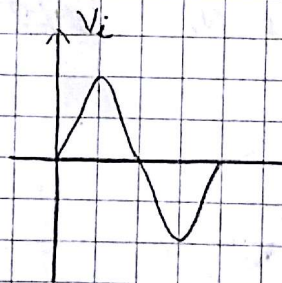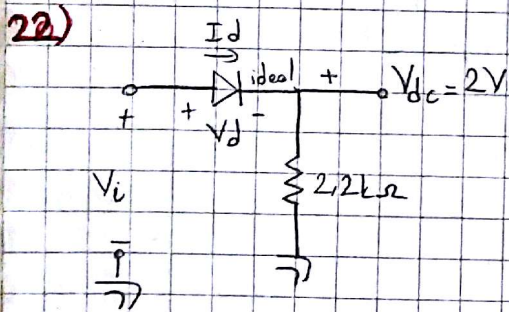

$$V_{dc} = 0.318 \cdot V_m$$

$$V_m = \frac{V_{dc}}{0.318} = 6.28$$

$$I_m = \frac{V_m}{R} = \frac{6.28}{2.2k} = 2.85A$$

